

4-bit CLA Adder

VLSI Course Project

1st Vignesh Vembar
ECE, IIIT Hyderabad
2023102019
vigneshvembar.m@students.iiit.ac.in

Abstract—This document is a report on the Design and Simulation of a 4-bit Carry Look Ahead Adder.

C. Full Circuit

I. INTRODUCTION

The Carry Look Ahead Adder is a digital circuit that is used to add two 4 bit binary numbers. It is faster than the Ripple Carry Adder as it generates the carry signals for all the bits at the same time.

IV. NGSPICE SIMULATION

A. Inverter

II. PROPOSED DESIGN

A. CLA Adder

B. D Flip Flop

III. VERILOG SIMULATION

A. CLA Adder



Fig. 1: GTKWave Plot of CLA Adder Verilog Simulation

B. D Flip Flop



Fig. 2: GTKWave Plot of D Flip Flop Verilog Simulation



 


Fig. 3: NGSPICE Plot of Inverter


B. NAND Gate

 


(a) 2 Input NAND

 

(b) 3 Input NAND

 


(c) 4 Input NAND

 


(d) 5 Input NAND

Fig. 4: NGSPICE Plot of NAND Gates


C. NOR Gate

 


(a) 2 Input NOR

 

(b) 3 Input NOR

 

(c) 4 Input NOR

 

(d) 5 Input NOR

Fig. 5: NGSPICE Plot of NOR Gates

D. XOR Gate

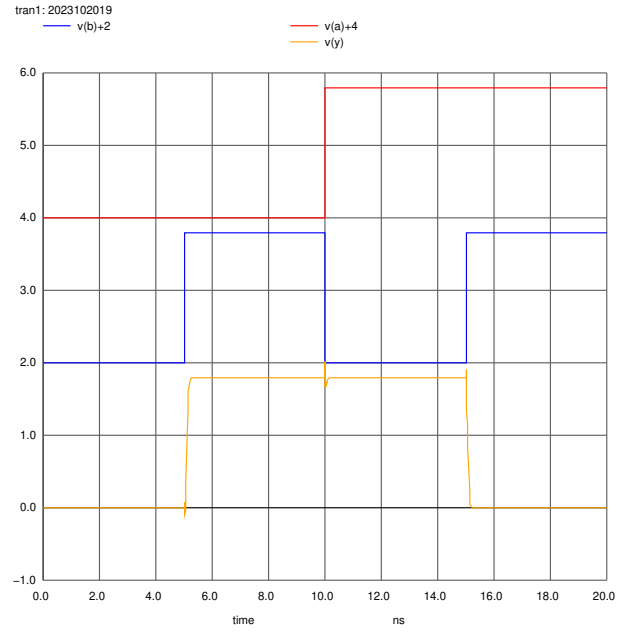


Fig. 6: NGSPICE Plot of CMOS XOR Gate

1) CMOS Implementation:

 


Fig. 7: NGSPICE Plot of CPTL XOR Gate

2) Complimentary Pass Transistor Implementation:

E. Propagate/Generate Generator

 


Fig. 8: NGSPICE Plot of CMOS Propagate/Generate Generator

1) CMOS Implementation:

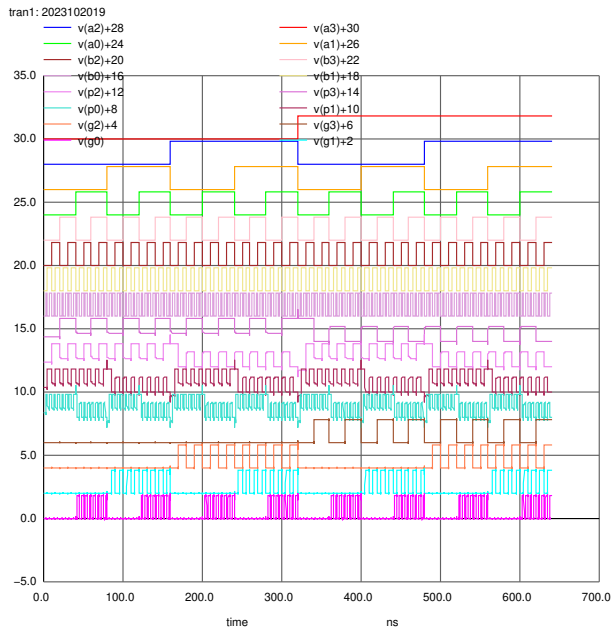


Fig. 9: NGSPICE Plot of CPTL Propagate/Generate Generator

2) Complimentary Pass Transistor Implementation:

F. Carry Look Ahead Generator

 


Fig. 10: NGSPICE Plot of CMOS Carry Look Ahead Generator

G. Sum Generator

 


Fig. 11: NGSPICE Plot of CMOS Sum Generator

1) CMOS Implementation:

 


Fig. 12: NGSPICE Plot of CPTL Sum Generator

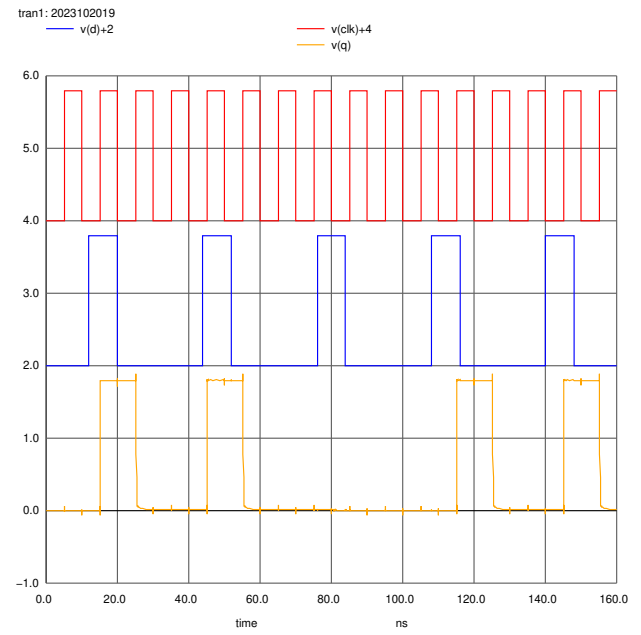


Fig. 14: NGSPICE Plot of Optimized D Flip Flop

2) Complimentary Pass Transistor Implementation:

H. D Flop Flop

2) Optimized Implementation:

I. Full Circuit

 


Fig. 13: NGSPICE Plot of CMOS D Flip Flop

 


Fig. 15: NGSPICE Plot of CMOS Circuit

1) CMOS Implementation:

1) CMOS Implementation:

 


Fig. 16: NGSPICE Plot of Optimized Circuit

2) Optimized Implementation:

V. MAGIC LAYOUT

A. Inverter

 


Fig. 17: MAGIC Layout of CMOS Inverter

B. NAND Gate

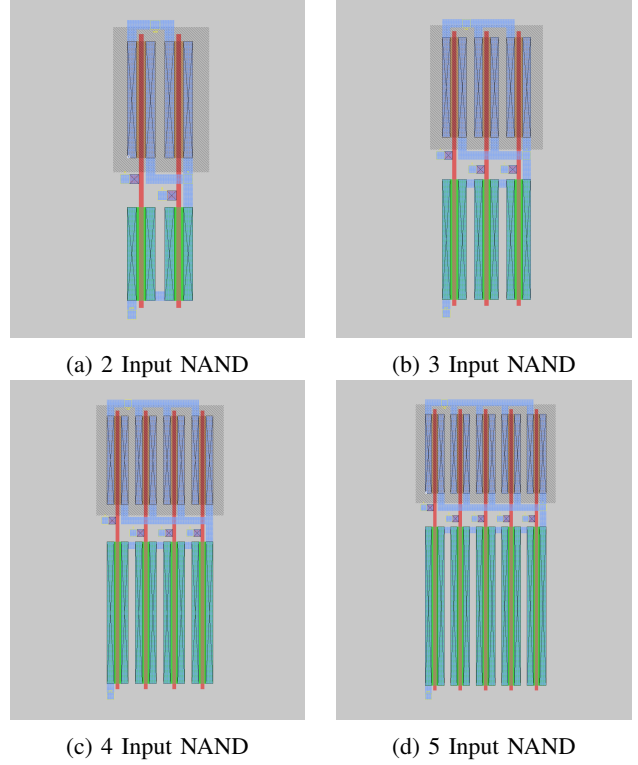


Fig. 18: MAGIC Layout of NAND Gates

C. NOR Gate

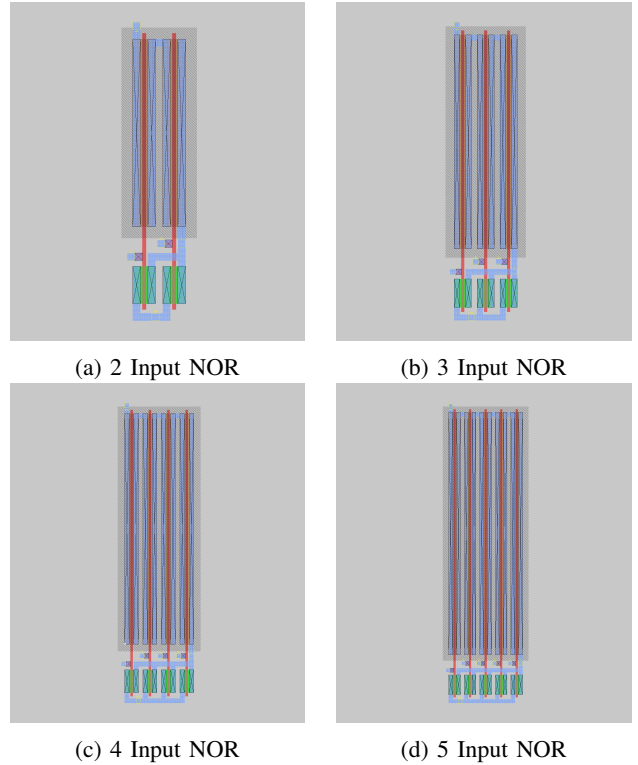


Fig. 19: MAGIC Layout of NOR Gates

- D. XOR Gate*
- E. Propagate/Generate Generator*
- F. Carry Look Ahead Generator*
- G. Sum Generator*
- H. D Flop Flop*
- I. Full Circuit*

VI. POST LAYOUT SIMULATION

- A. Inverter*
- B. NAND Gate*
- C. NOR Gate*
- D. XOR Gate*
- E. Propagate/Generate Generator*
- F. Carry Look Ahead Generator*
- G. Sum Generator*
- H. D Flop Flop*
- I. Full Circuit*

VII. FPGA SIMULATION

ACKNOWLEDGMENT

REFERENCES

- [1]